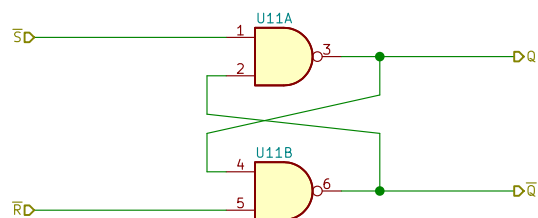


RS Latch




\overline{R}	\overline{S}	Q	\overline{Q}
0	0	1	1
0	1	0	1
1	0	1	0
1	1	Q	Q

(illegal state!)

(no change)


Gated RS Latch

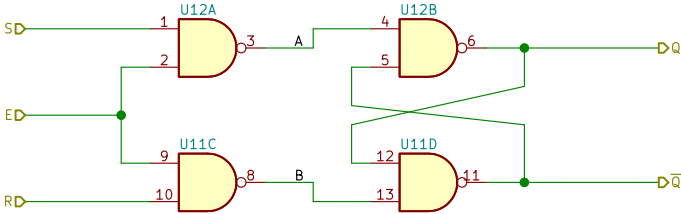


R	S	E	Q	\bar{Q}
X	X	0	Q	\bar{Q}
0	0	1	Q	\bar{Q}
0	1	1	1	0
1	0	1	0	1
1	1	1	1	1

Similar to RS but Q can only change when E is 1

D Flip Flop (Edge Triggered)

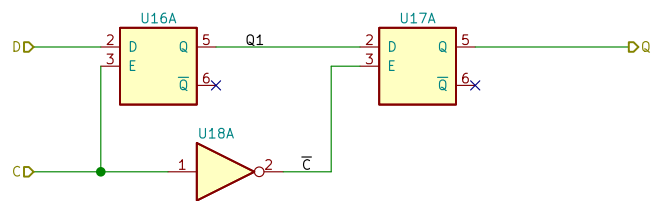

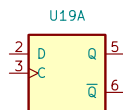Q can only change at the point in time
when C transitions from high to low.
We say "Q changes on the falling/trailing edge of C"



Symbol for a D Flip Flop

Copyright (C) 2019 John Winans	
This documentation describes Open Hardware and is licensed under the CERN OHL v. 1.2.	
You may redistribute and modify this documentation under the terms of the CERN OHL v.1.2. (http://ohwr.org/cernohl). This documentation is distributed WITHOUT ANY EXPRESS OR IMPLIED WARRANTY, INCLUDING OF MERCHANTABILITY, SATISFACTORY QUALITY AND FITNESS FOR A PARTICULAR PURPOSE. Please see the CERN OHL v.1.2 for applicable conditions	
If you chose to manufacture products based on this design, please notify me (see license section 4.2) via john@winans.org	
Sheet: /DFlipFlop/ File: DFlipFlop.sch	
Title: D Flip Flop (Edge Triggered)	
Size: USLetter	Date: 2020-02-18
KiCad E.D.A. kicad 5.1.5+dfsg1-2build2	Rev: 1.5
	Id: 4/4